

## 5 (1. Halbttag) | Operationsverstärker

Angelo Brade<sup>\*1</sup> and Jonas Wortmann<sup>†1</sup>

<sup>1</sup>Rheinische Friedrich–Wilhelms–Universität Bonn

September 7, 2024

---

<sup>\*</sup>s72abrad@uni-bonn.de

<sup>†</sup>s02jwort@uni-bonn.de

# Contents

<b>1</b>	<b>Introduction</b>	<b>1</b>
<b>2</b>	<b>Theory</b>	<b>1</b>
<b>3</b>	<b>Preliminary Tasks</b>	<b>1</b>
3.1	A . . . . .	1
3.2	B . . . . .	1
3.3	C . . . . .	1
3.4	D . . . . .	1
3.5	E . . . . .	2
<b>4</b>	<b>Auswertung</b>	<b>3</b>

## 1 Introduction

## 2 Theory

## 3 Preliminary Tasks

### 3.1 A

The equation hold

$$\frac{1}{\nu} = \frac{1}{\nu_0} + k \quad \nu = \frac{1}{\frac{1}{\nu_0} + k}. \quad (3.1)$$

For  $k = 0.1$ ,  $\nu_0 = 10^4$  and  $\nu_0 = 10^5$

$$\nu_1 \approx 9.990 \quad \nu_2 \approx 9.999. \quad (3.2)$$

The approximation  $\nu = \frac{1}{k}$  results in

$$\nu_{\text{Näh}} = 10. \quad (3.3)$$

The deviation of  $\nu_1$  and  $\nu_2$  from  $\nu_{\text{Näh}}$  lie at 0.001% and 0.0001% respectively.

### 3.2 B

It hold

$$\begin{aligned} U_x &= U_{\text{in}} - kU_{\text{out}} \\ \Leftrightarrow &= U_{\text{in}} - kv_0U_x \\ \Leftrightarrow &= \frac{U_{\text{in}}}{1 + v_0k}. \end{aligned} \quad (3.4) \quad (3.5)$$

For  $k = 0.1$ ,  $v_0 = 10^5$  and  $U_{\text{in}} = 1 \text{ V}$

$$U_x \approx 0.0001 \text{ V}. \quad (3.6)$$

### 3.3 C

Let there be a common mode signal with  $\Delta U_+ = \Delta U_- = +\Delta U_{\text{in}}$ . then

$$\Delta U_+ = \Delta U_E + \Delta U_1 \quad \Delta U_- = \Delta U_E + \Delta U_1. \quad (3.7)$$

from this follows  $\Delta U_{\text{in}} = \Delta U_E + \Delta U_1$ . The output voltage is

$$\Delta U_{\text{out}} = R_C \cdot \Delta I_C. \quad (3.8)$$

At point 1,

$$I_1 = 2I_E. \quad (3.9)$$

Therefore

$$\begin{aligned} \Delta U_{\text{in}} &= R_E \cdot \Delta I_E + R_1 \cdot 2\Delta I_E \\ &= \Delta I_E (R_E + 2R_1) \approx \Delta I_E \cdot 2R_1. \end{aligned} \quad (3.10)$$

At the node  $U_{\text{out}}$  applies

$$\Delta I_E = \Delta I_C \Rightarrow \Delta U_{\text{out}} = R_C \cdot \Delta I_E. \quad (3.11)$$

The amplification results in

$$v_{CM} = \frac{\Delta U_{\text{out}}}{\Delta U_{\text{in}}} = \frac{R_C}{2R_1}. \quad (3.12)$$

The common mode suppression is

$$10 \log \left( \frac{R_E}{R_1} \right) = 10 \log \left( \frac{1 \text{ k}\Omega}{100 \text{ k}\Omega} \right) = -20 \text{ dB}. \quad (3.13)$$

### 3.4 D

The frequency dependence of the impedance of a capacitor is

$$Z_1 = \frac{1}{i\omega C} = \frac{1}{i2\pi fC} \quad (3.14)$$

$$|Z_1| = \left| \frac{1}{i\omega C} \right| = \frac{1}{2\pi fC}. \quad (3.15)$$

The gain as a function of frequency is

$$v(f) = 1 + \frac{Z_2}{|Z_1|} = 1 + R2\pi fC. \quad (3.16)$$

The limits are

$$\lim_{f \rightarrow 0} [1 + R2\pi fC] = 1 \quad \lim_{f \rightarrow \infty} [1 + R2\pi fC] = \infty. \quad (3.17)$$

For  $|Z_1| = R$  it has to hold that

$$\frac{1}{2\pi fC} = R \Leftrightarrow f = \frac{1}{2\pi RC}. \quad (3.18)$$

With concrete values  $Z_1 = R = 100 \text{ k}\Omega$  and  $Z_1 = C = 100 \text{ nF}$ , the frequency is

$$f = \frac{1}{2\pi RC} \approx 15.92 \text{ Hz} \Rightarrow v(f) \approx 2. \quad (3.19)$$

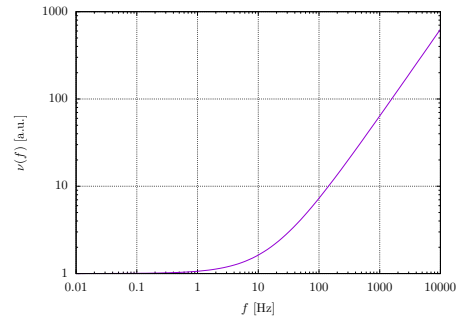


Figure 1: Time dependend amplification of a non-invertible amplifier as a BODE-plot

### 3.5 E

Let

$$v = \frac{U_{\text{out}}}{U_{\text{in}}} = -\frac{Z_2}{Z_1}. \quad (3.20)$$

The minus sign results from the negative feedback. Because of the golden rule  $U_- = U_+ = 0 \text{ V}$ , the negative feedback has a different sign compared to the input signal.

The input impedance is very high and the output impedance very low.

## 4 Auswertung

## List of Figures

1	Time dependend amplification of a non-invertible amplifier as a BODE-plot . . . . .	1
---	---	---

## List of Tables

## Source