

5 (1. Halbttag) | Operationsverstärker

Angelo Brade^{*1} and Jonas Wortmann^{†1}

¹Rheinische Friedrich–Wilhelms–Universität Bonn

September 11, 2024

^{*}s72abrad@uni-bonn.de

[†]s02jwort@uni-bonn.de

Contents

1	Introduction	1
2	Theory	1
3	Preliminary Tasks	2
3.1	A	2
3.2	B	2
3.3	C	2
3.4	D	3
3.5	E	3
3.6	F	3
3.7	G	3
3.8	H	3
3.9	I	3
3.10	J	4
3.11	K	4
4	Analysis	5
4.1	Non-inverting amplifier	5

1 Introduction

This experiment deals with the opamp and its functionality in different circuits. The opamp can be used as a non-inverting amplifier, adder, differential amplifier, current source, monoflop, to logarithmize or exponentiate and to differentiate or integrate a signal. It is also possible to build a SCHMITT-trigger or an astable multivibrator. In this experiment the opamp will serve as a non-inverting amplifier, adder, current source, integrator and differential amplifier.

2 Theory

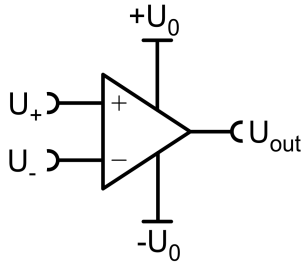


Figure 1: Schematic of an opamp; Abb. 5/6.1[1]

The most important properties of opamps are

- With stable negative feedback, the opamp regulates the output voltage such that $U_+ = U_-$.
- There is close to no input current $I_+ = I_- \approx 0$.

Important features of real opamps to keep in mind

- The maximum output voltage can't be higher than the maximum supply voltage.
- Due to internal constraints, the opamp has a finite slew rate, meaning that it can't change a signal at infinite speed.
- The open-loop gain decreases with rising frequency. The bandwidth is the cutoff frequency at which $\nu = \frac{1}{\sqrt{2}}$.
- For $U_+ = U_- = 0$ one would assume that $U_{out} = 0$. In real world opamps this is not the case. The output voltage goes to zero at a certain difference between U_+ and U_- . This difference is component specific.
- The output voltage should not change if both input voltages increase at the same rate. This is not the case in the real world. The common mode rejection ratio is the ratio between the differential gain and common mode gain.

The opamp can be utilised as a non-inverting amplifier with an ideal open-loop gain of infinity. Here $U_- = k \cdot U_{out}$ and $U_+ = U_{in}$. The gain is

$$\nu = \frac{U_{out}}{U_{in}} = \frac{1}{k} = 1 + \frac{Z_2}{Z_1}. \quad (2.1)$$

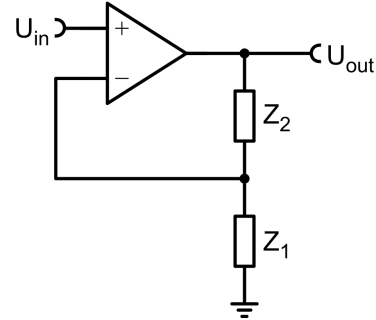


Figure 2: Non-inverting amplifier; Abb. 5/6.4[1]

The opamp can also be used as an adder. As discussed in [preliminary task F](#) the output voltage is an addition of input voltages

$$U_{out} = c_i U_i \quad c_i = -\frac{R_0}{R_i}. \quad (2.2)$$

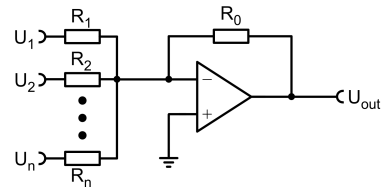


Figure 3: Adder; Abb. 5/6.6[1]

The opamp can also integrate signals by charging a capacitor to sum up the input signal

$$U_{out}(t) = -\frac{1}{R_1 C} \int_{t_0}^t U_{in}(t') dt'. \quad (2.3)$$

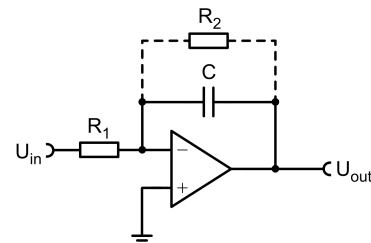


Figure 4: Integrator; Abb. 5/6.11[1]

At last the opamp is used in a circuit to function as a differential amplifier. As discussed in [preliminary task G](#),

the output voltage is an amplification of the difference of the input voltages

$$U_{\text{out}} = \frac{R_2}{R_1} (U_2 - U_1). \quad (2.4)$$

Here $\frac{R_2}{R_1}$ is the gain.

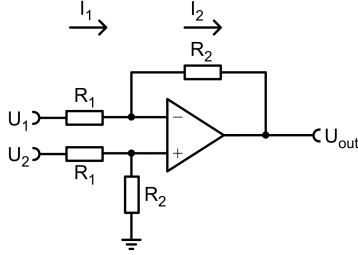


Figure 5: Differential amplifier; Abb. 5/6.7[1]

When using the opamp as an inverting amplifier, the current flowing through the negative feedback circuit does not depend on Z_2 but only on U_{in} and Z_1 . Thus one can construct a current source for the resistance Z_2 which can be controlled via the input voltage.

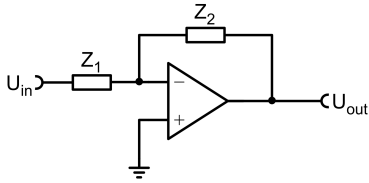


Figure 6: Inverting amplifier; Abb. 5/6.5[1]

The astable multivibrator uses the SCHMITT-trigger to construct a signal from an ideal wave form, see [preliminary task K](#).

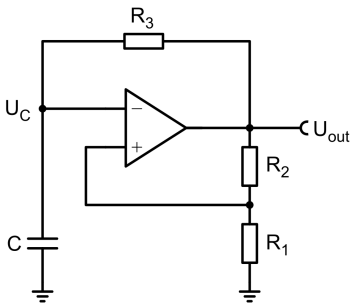


Figure 7: Astable multivibrator; Abb. 5/6.15[1]

3 Preliminary Tasks

3.1 A

The equation hold

$$\frac{1}{\nu} = \frac{1}{\nu_0} + k \quad \nu = \frac{1}{\frac{1}{\nu_0} + k}. \quad (3.1)$$

For $k = 0.1$, $\nu_0 = 10^4$ and $\nu_0 = 10^5$

$$\nu_1 \approx 9.990 \quad \nu_2 \approx 9.999. \quad (3.2)$$

The approximation $\nu = \frac{1}{k}$ results in

$$\nu_{\text{Näh}} = 10. \quad (3.3)$$

The deviation of ν_1 and ν_2 from $\nu_{\text{Näh}}$ lie at 0.001% and 0.0001% respectively.

3.2 B

It hold

$$U_x = U_{\text{in}} - kU_{\text{out}} \quad (3.4)$$

$$\Leftrightarrow U_x = U_{\text{in}} - kv_0 U_x$$

$$\Leftrightarrow U_x = \frac{U_{\text{in}}}{1 + v_0 k}. \quad (3.5)$$

For $k = 0.1$, $v_0 = 10^5$ and $U_{\text{in}} = 1 \text{ V}$

$$U_x \approx 0.0001 \text{ V}. \quad (3.6)$$

3.3 C

Let there be a common mode signal with $\Delta U_+ = \Delta U_- = +\Delta U_{\text{in}}$. then

$$\Delta U_+ = \Delta U_E + \Delta U_1 \quad \Delta U_- = \Delta U_E + \Delta U_1. \quad (3.7)$$

from this follows $\Delta U_{\text{in}} = \Delta U_E + \Delta U_1$. The output voltage is

$$\Delta U_{\text{out}} = R_C \cdot \Delta I_C. \quad (3.8)$$

At point 1,

$$I_1 = 2I_E. \quad (3.9)$$

Therefore

$$\begin{aligned} \Delta U_{\text{in}} &= R_E \cdot \Delta I_E + R_1 \cdot 2\Delta I_E \\ &= \Delta I_E (R_E + 2R_1) \approx \Delta I_E \cdot 2R_1. \end{aligned} \quad (3.10)$$

At the node U_{out} applies

$$\Delta I_E = \Delta I_C \Rightarrow \Delta U_{\text{out}} = R_C \cdot \Delta I_E. \quad (3.11)$$

The amplification results in

$$v_{CM} = \frac{\Delta U_{out}}{\Delta U_{in}} = \frac{R_C}{2R_1}. \quad (3.12)$$

The common mode suppression is

$$10 \log \left(\frac{R_E}{R_1} \right) = 10 \log \left(\frac{1 \text{ k}\Omega}{100 \text{ k}\Omega} \right) = -20 \text{ dB}. \quad (3.13)$$

3.4 D

The frequency dependence of the impedance of a capacitor is

$$Z_1 = \frac{1}{i\omega C} = \frac{1}{i2\pi fC} \quad (3.14)$$

$$|Z_1| = \left| \frac{1}{i\omega C} \right| = \frac{1}{2\pi fC}. \quad (3.15)$$

The gain as a function of frequency is

$$v(f) = 1 + \frac{Z_2}{|Z_1|} = 1 + R2\pi fC. \quad (3.16)$$

The limits are

$$\lim_{f \rightarrow 0} [1 + R2\pi fC] = 1 \quad \lim_{f \rightarrow \infty} [1 + R2\pi fC] = \infty. \quad (3.17)$$

For $|Z_1| = R$ it has to hold that

$$\frac{1}{2\pi fC} = R \Leftrightarrow f = \frac{1}{2\pi RC}. \quad (3.18)$$

With concrete values $Z_1 = R = 100 \text{ k}\Omega$ and $Z_1 = C = 100 \text{ nF}$, the frequency is

$$f = \frac{1}{2\pi RC} \approx 15.92 \text{ Hz} \Rightarrow v(f) \approx 2. \quad (3.19)$$

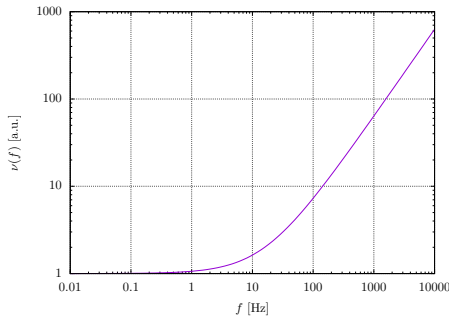


Figure 8: Time dependend amplification of a non-invertible amplifier as a BODE-plot

3.5 E

Let

$$v = \frac{U_{out}}{U_{in}} = -\frac{Z_2}{Z_1}. \quad (3.20)$$

The minus sign results from the negative feedback. Because of the golden rule $U_- = U_+ = 0 \text{ V}$, the negative feedback has a different sign compared to the input signal.

The input impedance is very high and the output impedance very low.

3.6 F

The first KIRCHHOFF's law states (EINSTEIN notation)

$$\sum_i I_i = -I_{out} \quad (3.21)$$

$$\Leftrightarrow \frac{U_i}{R_i} = -\frac{U_{out}}{R_0} \quad (3.22)$$

$$\Leftrightarrow -\frac{R_0}{R_i} U_i = U_{out} \quad (3.23)$$

$$\Leftrightarrow c_i U_i = U_{out}. \quad (3.24)$$

3.7 G

$$U_+ = U_2 \frac{R_2}{R_1 + R_2} \quad |\text{voltage divider}| \quad (3.25)$$

$$U_- = U_+ \quad |\text{golden rule}| \quad (3.26)$$

$$I_1 = \frac{U_1 - U_-}{R_1} \quad |\text{OHM's law}| \quad (3.27)$$

$$I_2 = I_1 \quad |\text{golden rule}| \quad (3.28)$$

$$I_2 = \frac{U_- - U_{out}}{R_2} \quad |\text{OHM's law.}| \quad (3.29)$$

The final result $U_{out} = \frac{R_2}{R_1} (U_2 - U_1)$ can be calculated using the above relations.

3.8 H

A constant negative input voltage provides a continuous charge to the capacitor, resulting in a steadily rising output voltage. One could also argue that for a constant input voltage the integral will increase linearly.

3.9 I

For an inverting amplifier $\nu = -\frac{Z_2}{Z_1}$. With $Z_1 = R$ and $Z_2 = \frac{1}{i\omega C}$

$$\nu = -\frac{1}{i\omega CR}. \quad (3.30)$$

The phase relation between the output- and input signal is then

$$\tan \Phi = \frac{\Im(\nu)}{\Re(\nu)} = \lim_{\alpha \rightarrow 0} \frac{-\frac{1}{\omega CR}}{\alpha} = -\infty. \quad (3.31)$$

Thus $\Phi = -\frac{\pi}{2}$.

3.10 J

The AD711 opamp has a slew rate of $s = 20 \text{ V } \mu\text{s}^{-1}$. The peak to peak voltage lies at $U_{pp} = 28 \text{ V}$. This means that the AD711 needs

$$t = \frac{U_{pp}}{s} = 1.4 \mu\text{s} \quad (3.32)$$

to get from -14 V to 14 V . The switching frequency is therefore

$$\frac{1}{t} = 0.714 \mu\text{s}^{-1}. \quad (3.33)$$

3.11 K

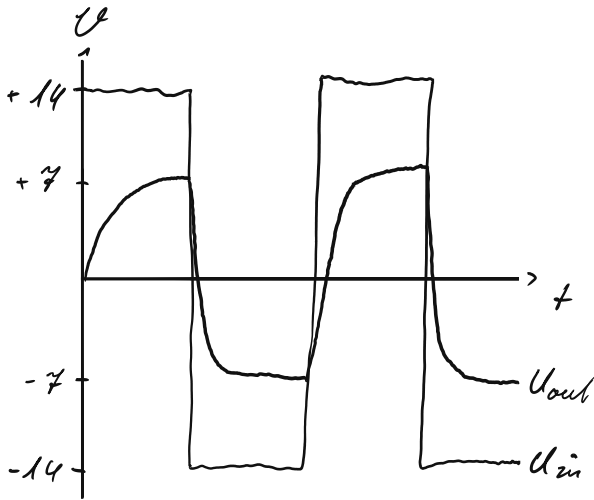


Figure 9: Astable multivibrator, voltage curve

The ideal signal is a square-wave with $U_{\max, \min} \pm 14 \text{ V}$. Due to the slew rate of the opamp, the signal need time to rise to $\pm 7 \text{ V}$. The output voltage can be modeled with an exponential function.

4 Analysis

4.1 Non-inverting amplifier

The [non-inverting amplifier](#) is built with a gain of $\nu = 11$ (i.e. $R_1 = 1 \text{ k}\Omega$ and $R_2 = 10 \text{ k}\Omega$). A signal of $U_{pp} = 1 \text{ V}$ is applied to the circuit and the gain is observed for different frequencies.

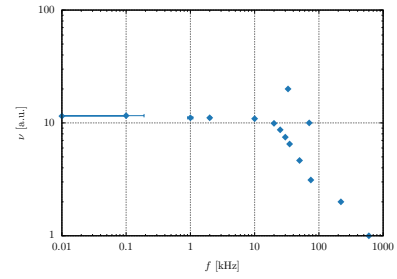


Figure 10: BODE-plot of a non-inverting amplifier with $\nu = 11$

List of Figures

1	Schematic of an opamp; Abb. 5/6.1[1]	1
2	Non-inverting amplifier; Abb. 5/6.4[1]	1
3	Adder; Abb. 5/6.6[1]	1
4	Integrator; Abb. 5/6.11[1]	1
5	Differential amplifier; Abb. 5/6.7[1]	2
6	Inverting amplifier; Abb. 5/6.5[1]	2
7	Astable multivibrator; Abb. 5/6.15[1]	2
8	Time dependend amplification of a non-invertible amplifier as a BODE-plot	3
9	Astable multivibrator, voltage curve	4
10	BODE-plot of a non-inverting amplifier with $\nu = 11$	5

List of Tables

Source

- [1] Fabian Hügging. *Elektronik-Praktikum Versuchsanleitung*. Universität Bonn, kurs b edition, 2024.